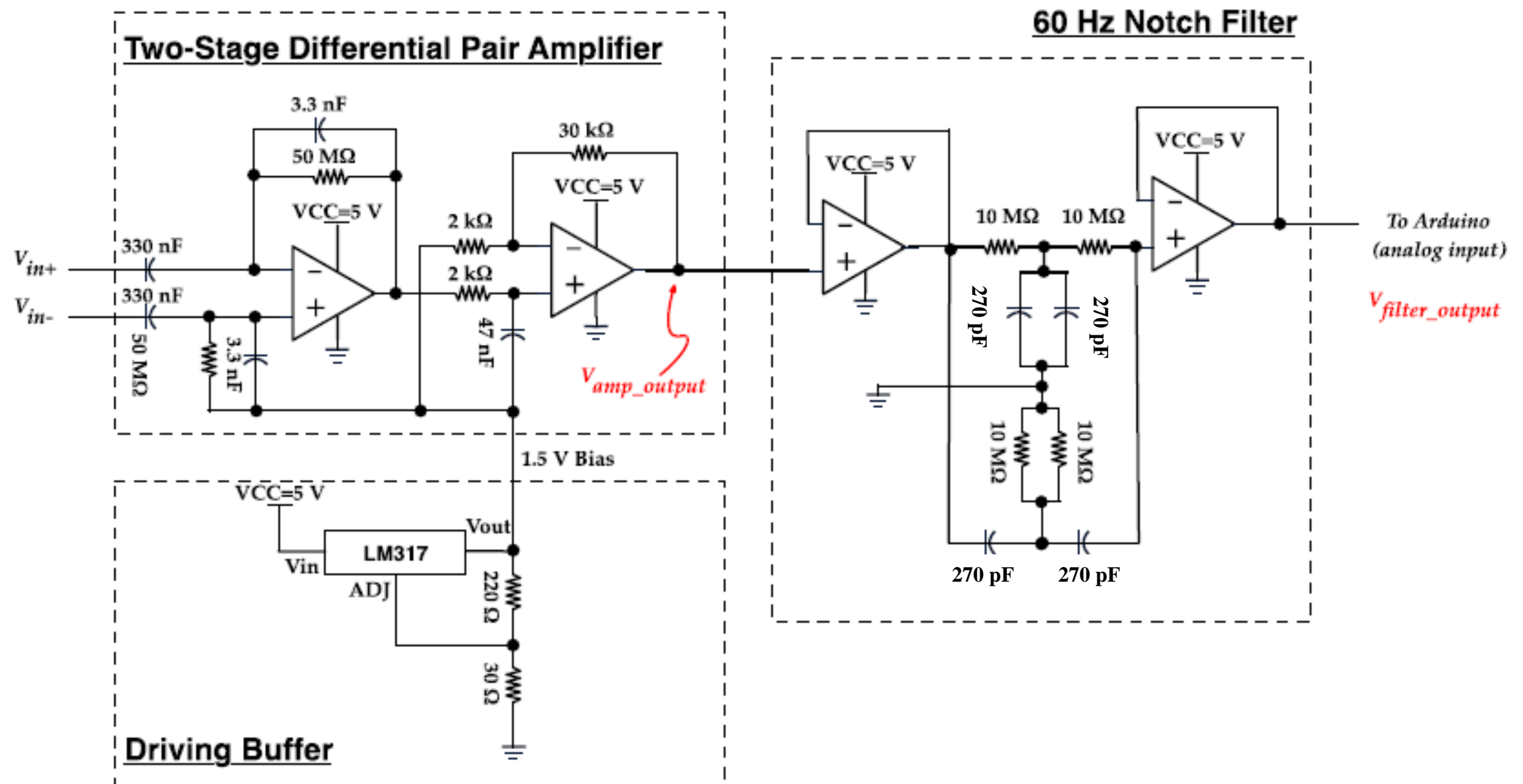


ECG Circuit


ECG Circuit




Debug

- Driving Buffer -> 1.5V Bias
- First Stage Amplifier -> gain = 100
- Second Stage Amplifier -> gain = 15
- 60 Hz Notch Filter

Electrodes

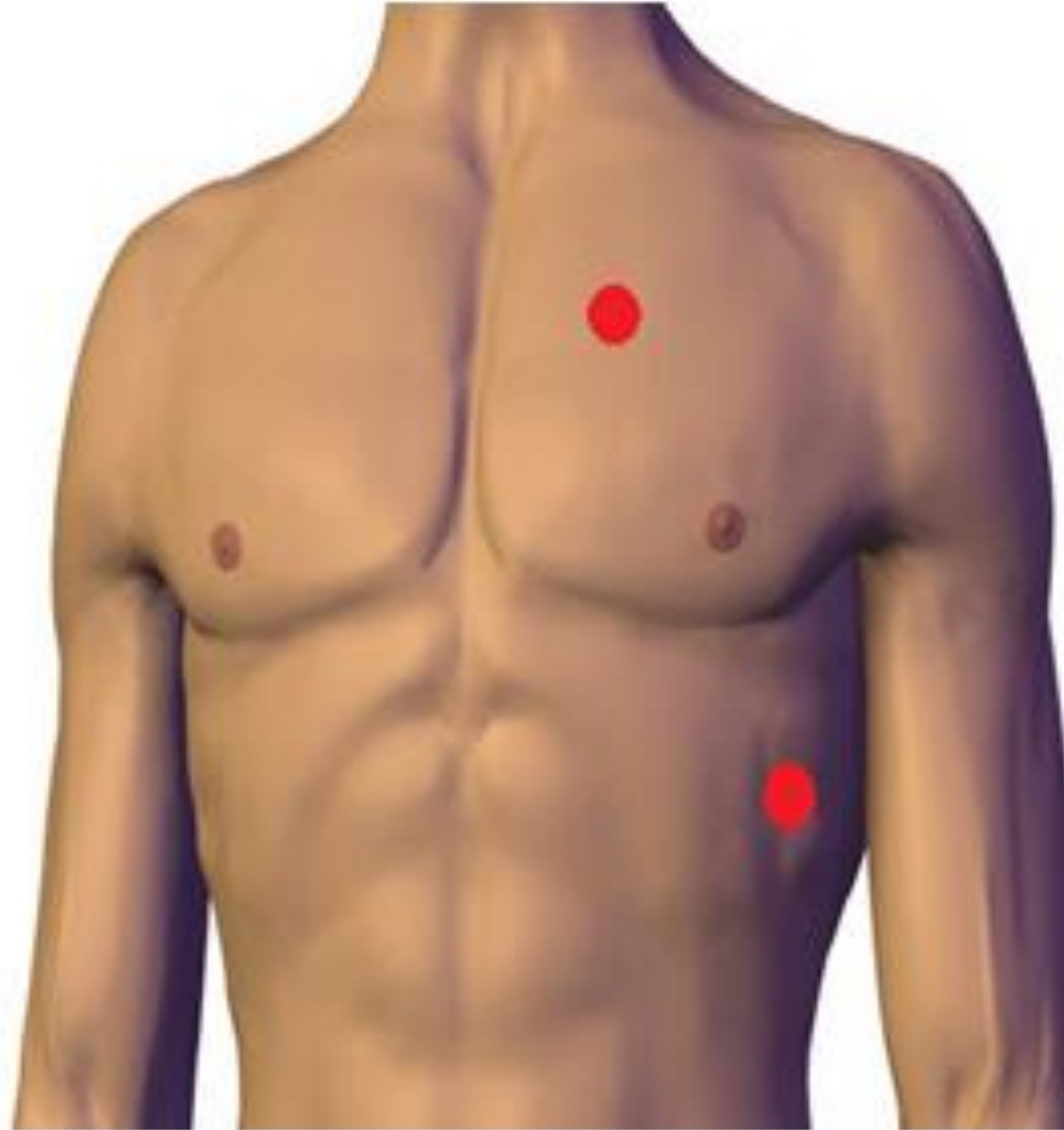

ECG Circuit

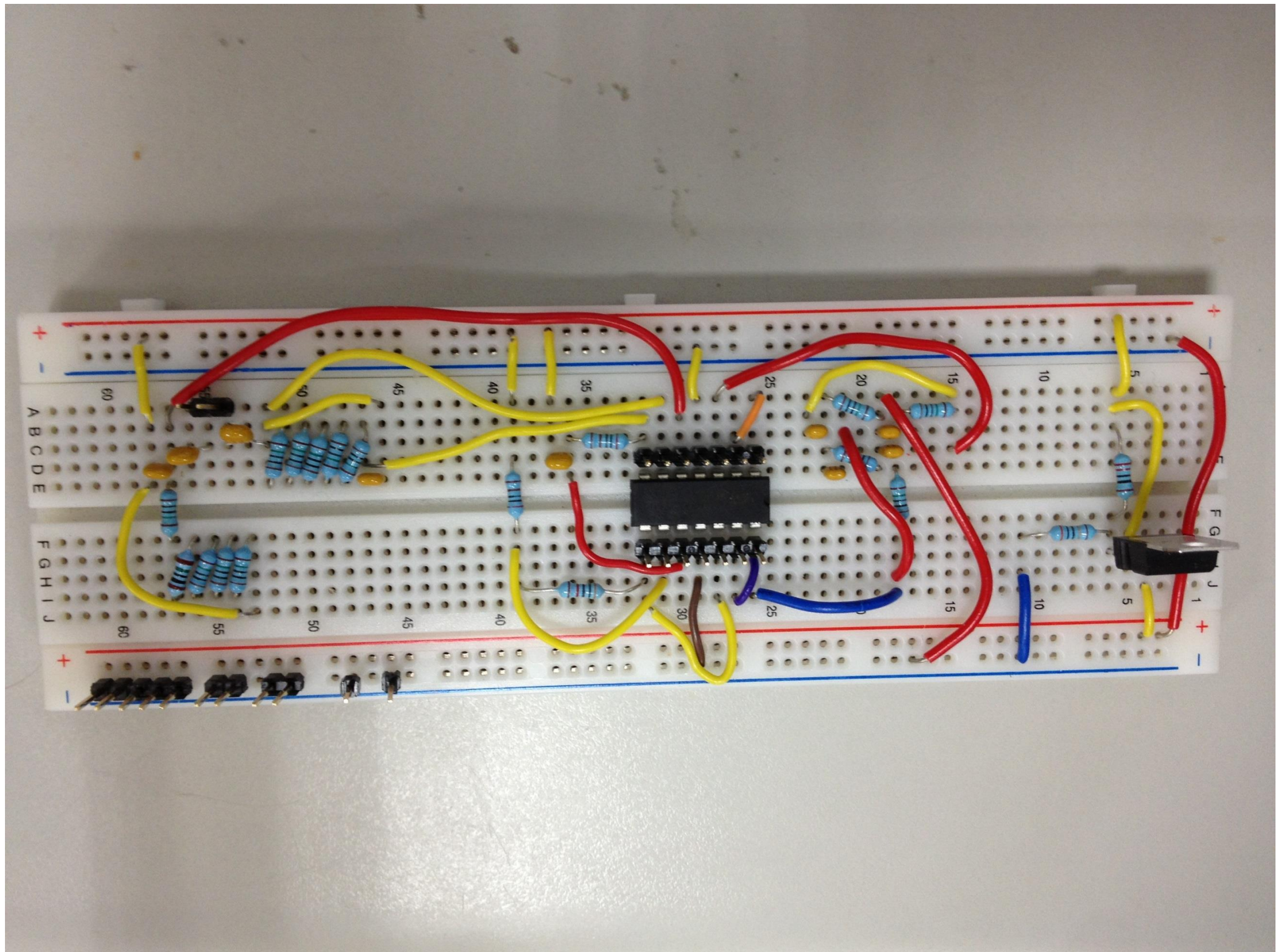

ECG Circuit

